
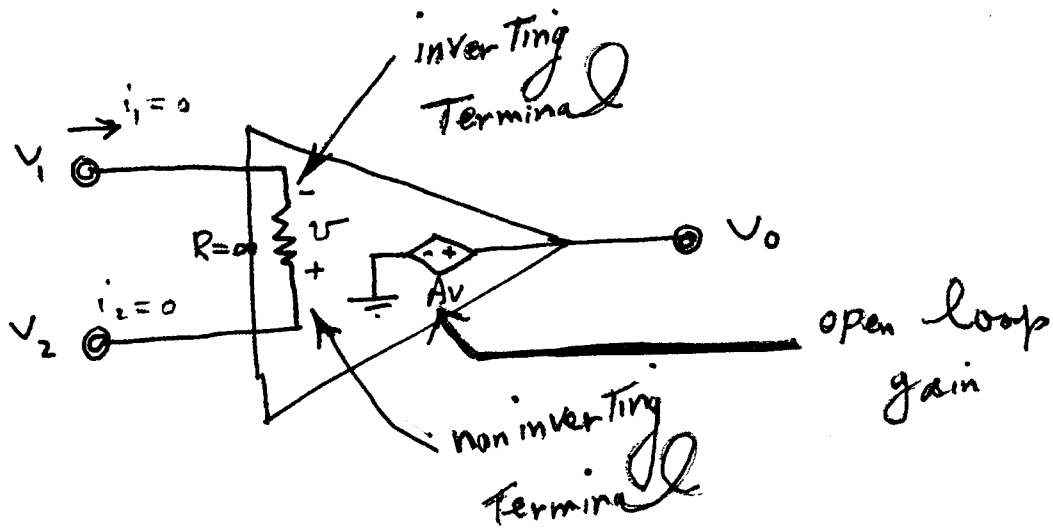


the operational Amplifier - chapter 6

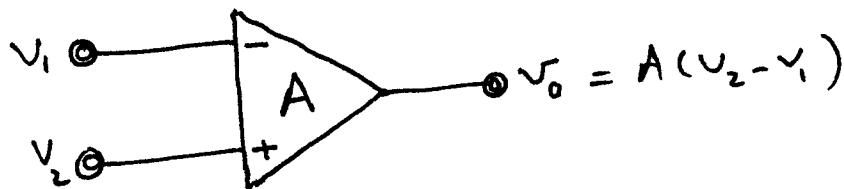


$$v_0 = A v = A (v_2 - v_1)$$

the ideal amp is modeled as follows:



The inverting configuration

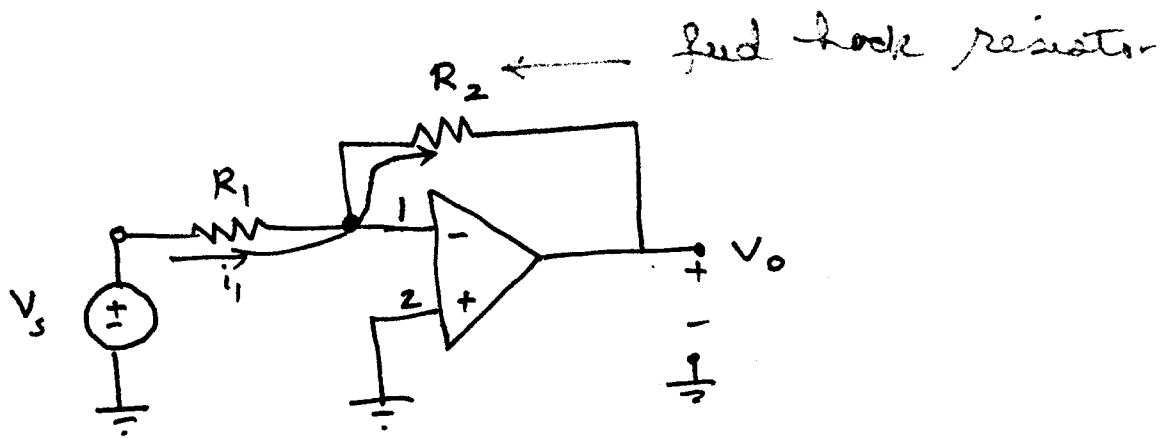

KCL:

$$\frac{V_s - V_1}{R_1} = \frac{V_1 - V_o}{R_2} \quad (1)$$

But $V_o = A(V_2 - V_1) \Rightarrow V_2 - V_1 = \frac{V_o}{A} \rightarrow 0$ ($V_2 =$

$$\therefore V_2 = V_1 = 0 \quad (2)$$

\therefore (2) in (1) \Rightarrow


$$\frac{V_s}{R_1} = -\frac{V_o}{R_2} \Rightarrow V_o = \left(-\frac{R_2}{R_1}\right)V_s$$

closed loop gain < 0

note:

Although $A \rightarrow \infty$, for a finite V_s , V_o is finite ($R_1 \neq 0$).

The noninverting configuration

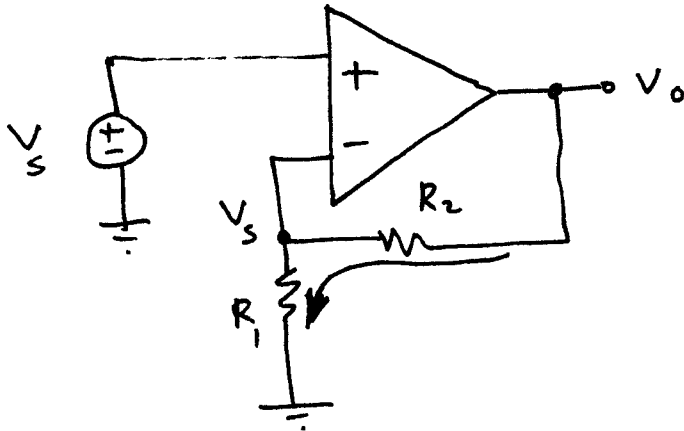


$$\frac{V_o - V_s}{R_2} = \frac{V_s}{R_1} \Rightarrow V_o = \left(\frac{R_2}{R_1} + 1 \right) V_s$$


$$\therefore V_o = \left(\frac{R_1 + R_2}{R_1} \right) V_s$$

closed loop gain > 1 .

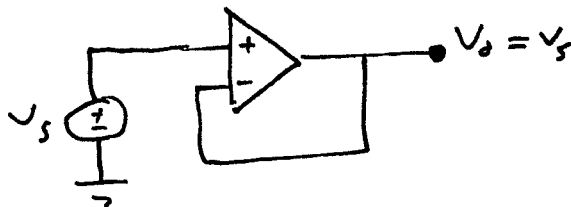if $R_2 = 0$ and $R_1 \rightarrow \infty \Rightarrow V_o = V_s$
and the circuit is called a voltage follower.



2.19 (Bobrow):
90

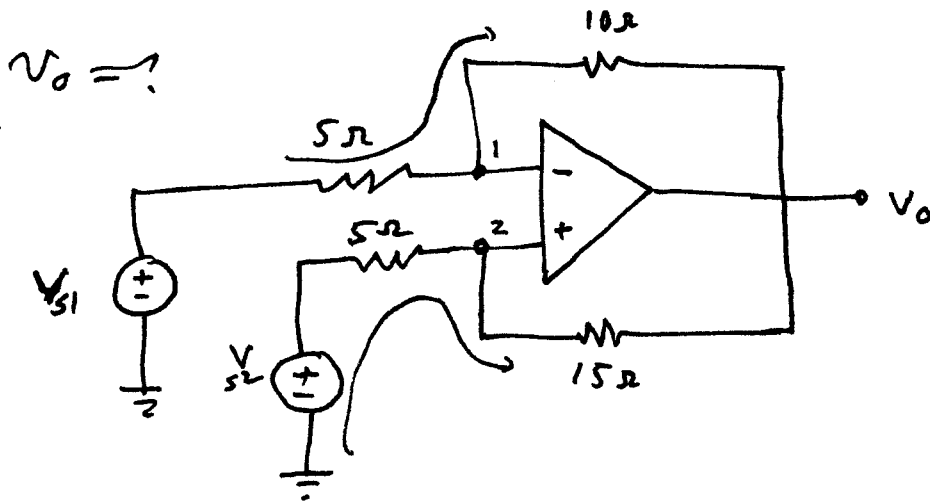

KCL 1.
$$\frac{V_{s1} - V_1}{5} = \frac{V_1 - V_0}{10} \quad (1)$$

KCL 2.
$$\frac{V_{s2} - V_2}{5} = \frac{V_2 - V_0}{15} \quad (2)$$

note that $V_1 = V_2 = V \neq 0$. (3)

(3) in (1) and (2) \Rightarrow


$$V_{s1} = \frac{1}{2}(V - V_0) + V = \frac{3}{2}V - \frac{1}{2}V_0 \quad (4)$$

$$V_{s2} = \frac{1}{3}(V - V_0) + V = \frac{4}{3}V - \frac{1}{3}V_0 \quad (5)$$

eliminate V from (4) and (5) \Rightarrow


$$\boxed{V_0 = -8V_{s1} + 9V_{s2}}$$

2.20 :
91

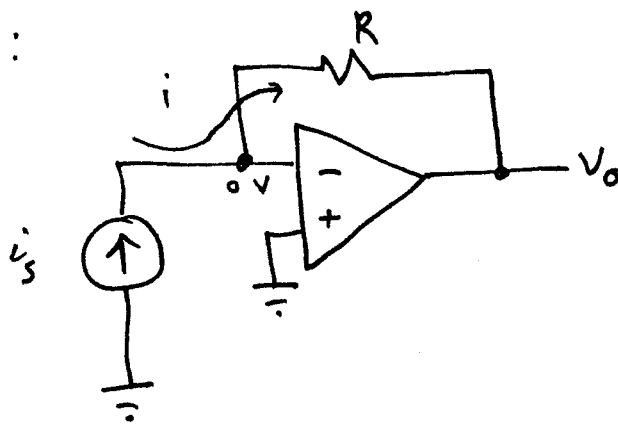

$$i_s = \frac{0 - V_o}{R} \Rightarrow \frac{V_o}{i_s} = -R$$

2.22 :
91

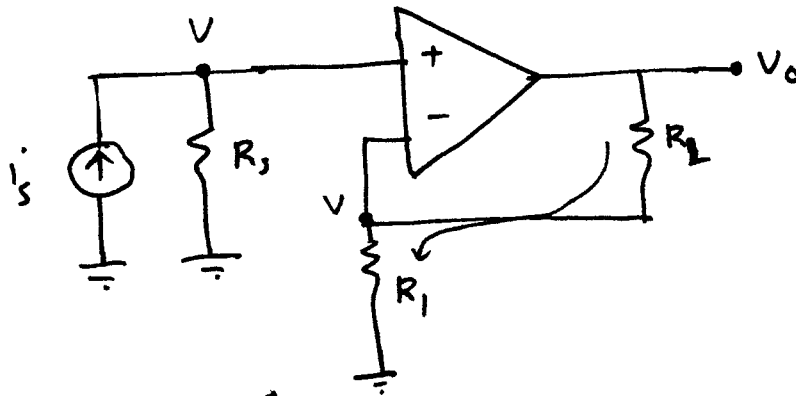

$$i_s = \frac{V}{R_s} \quad (1)$$

$$\frac{V_o - V}{R_L} = \frac{V}{R_1} \Rightarrow V_o = \frac{R_L}{R_1} V + V \quad (2)$$

$$\frac{(2)}{(1)} \Rightarrow \frac{V_o}{i_s} = \frac{\left(\frac{R_L}{R_1} + 1\right) V}{\frac{1}{R_s} V} = R_s \left(1 + \frac{R_L}{R_1}\right)$$