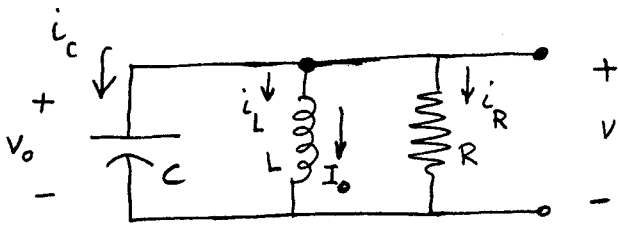


Chapter 8.

RLC Circuits

1. Natural response of Parallel RLC.



$$i_R + i_L + i_C = 0$$

$$\underbrace{\frac{v}{R}}_{i_R} + \underbrace{\frac{1}{L} \int_0^t v(\tau) d\tau}_{i_L} + I_0 + \underbrace{C \frac{dv}{dt}}_{i_C} = 0$$

$$\frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v + C \frac{d^2 v}{dt^2} = 0$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

$$v = A e^{st}, \quad \frac{dv}{dt} = A s e^{st}, \quad \frac{d^2 v}{dt^2} = A s^2 e^{st}$$

$$A s^2 e^{st} + \frac{1}{RC} A s e^{st} + \frac{A}{LC} e^{st} = 0$$

$$A e^{st} \left[s^2 + \frac{s}{RC} + \frac{1}{LC} \right] = 0$$

Characteristic eqⁿ

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$s_{1,2}$: Complex Freq.


α : Neper Freq.

ω_0 : Resonant radian Freq.

there are three cases:

1. $\alpha^2 - \omega_0^2 > 0 \Rightarrow \omega_0 < \alpha$ (overdamped)
↙ real, distinct roots
2. $\alpha^2 - \omega_0^2 < 0 \Rightarrow \omega_0 > \alpha$ (underdamped)
↙ complex conjugate roots
3. $\alpha^2 - \omega_0^2 = 0 \Rightarrow \omega_0 = \alpha$ (critically damped)
↙ two equal roots

8.1 :
268

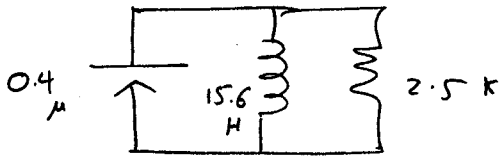

$$(a) \quad s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$s^2 + \frac{1}{(2.5)(0.4)(10^3)(10^{-6})} s + \frac{1}{(15.6)(0.4)(10^{-6})} = 0$$

$$s^2 + 1000s + 160000 = 0$$

$$s_{1,2} = -500 \pm \sqrt{(500)^2 - 160000} \begin{matrix} \nearrow -200 \\ \searrow -800 \end{matrix}$$

(b) overdamp

$$(c) \quad \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} = 500 \Rightarrow L = 5 \text{ H}$$

$$(d) \quad \left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} \Rightarrow R = 3125 \Omega$$

1. Overdamped Voltage Response : (s_1, s_2 are)
real - distinct

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$v(0) = v_0 \Rightarrow A_1 + A_2 = v_0$ (1)

also in

$$\frac{V}{R} + \frac{1}{L} \int_0^t v(\tau) d\tau + I_0 + C \frac{dv}{dt} = 0 \quad t \geq 0$$

at $t=0$ we have

$$\frac{v_0}{R} + I_0 + C \frac{dv(0)}{dt} = 0$$

initial
Conditions

$$\frac{dv(0)}{dt} = -\frac{v_0}{RC} - \frac{I_0}{C}$$

$$\left. \frac{dv}{dt} \right|_{t=0} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t} \Big|_{t=0} = A_1 s_1 + A_2 s_2$$

$$A_1 s_1 + A_2 s_2 = -\frac{v_0}{RC} - \frac{I_0}{C} \quad (2)$$

from (1) and (2)

$$\Rightarrow A_{1,2} = \pm \frac{v_0 s_{2,1} + \left(\frac{1}{C}\right) \left[\frac{v_0}{R} + I_0\right]}{s_2 - s_1}$$

2. Under damped voltage Response (s_1, s_2 Complex conjugate)

$$s_{1,2} = -\alpha \pm j \underbrace{\sqrt{N_0^2 - \alpha^2}}_{\omega_d}$$

ω_d : damped radian freq.

$$s^2 + \frac{1}{Rc}s + \frac{1}{Lc} = 0$$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$= A_1 e^{(-\alpha + j\omega_d)t} + A_2 e^{(-\alpha - j\omega_d)t}$$

$$= e^{-\alpha t} \left[A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t} \right]$$

$$= e^{-\alpha t} \left[A_1 (\cancel{C_1 \omega_d t} + j \sin \omega_d t) + A_2 (\cancel{C_2 \omega_d t} - j \sin \omega_d t) \right]$$

$$= e^{-\alpha t} \left[\underbrace{(A_1 + A_2)}_{B_1} C_3 \omega_d t + \underbrace{(A_1 j - A_2 j)}_{B_2} \sin \omega_d t \right]$$

Real part \downarrow

$$= e^{-\alpha t} \left[B_1 C_3 \omega_d t + B_2 \sin \omega_d t \right]$$

Imaginary part \downarrow

$$\text{But } \begin{cases} v(0) = V_0 \\ \frac{dv(0)}{dt} = -\frac{V_0}{RC} - \frac{I_0}{C} \end{cases}$$

$$\therefore \underline{\underline{B_0 = B_1}}$$

$$\left. \frac{dv}{dt} \right|_{t=0} = \omega_d B_2 - \cancel{\alpha B_1} = -\frac{V_0}{RC} - \frac{I_0}{C}$$

$$\therefore \underline{\underline{B_2 = -\frac{\alpha}{\omega_d} (V_0 + 2I_0 R)}}$$

$$\therefore v(t) = V_0 e^{-\alpha t} \cos \omega_d t - \frac{\alpha}{\omega_d} (V_0 + 2I_0 R) e^{-\alpha t} \sin \omega_d t //$$

3. Critically Damped Voltage Response :

$$(s_1 = s_2)$$

$$\therefore s_1 = s_2 = -\alpha s - \frac{1}{2RC}$$

$$v(t) = D_2 e^{s_1 t} + D_1 t e^{s_2 t}$$

$$= D_2 e^{-\alpha t} + D_1 t e^{-\alpha t}$$


$$v(0) = v_0 = D_2$$

$$v'(0) = -\frac{v_0}{RC} - \frac{I_0}{C} = D_1 - \alpha D_2$$

$$D_1 = -\alpha (v_0 + 2I_0 R)$$

$$\swarrow \alpha = \frac{1}{2RC}$$

Review :

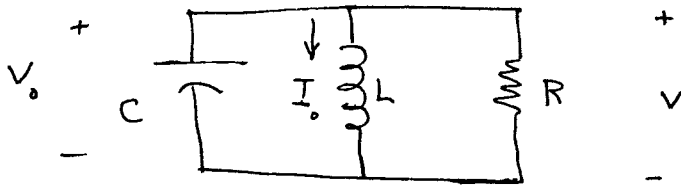

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0.$$

$$v(0) = v_0, \quad v'(0) = -\frac{1}{C} \left(\frac{v_0}{R} + I_0 \right)$$

} ← I.V.P

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0.$$

① $s_{1,2}$ real, distinct


(overdamped)

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

where

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$
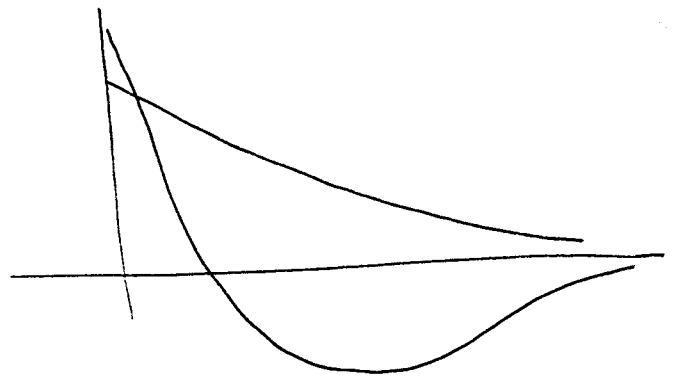
$$\begin{cases} \alpha = \frac{1}{2RC} \\ \omega_0 = \frac{1}{\sqrt{LC}} \end{cases}$$




(b) $s_{1,2}$ complex conjugate (under damped)

$$V(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$


where

$$s_{1,2} = -\alpha \pm j \omega_d$$
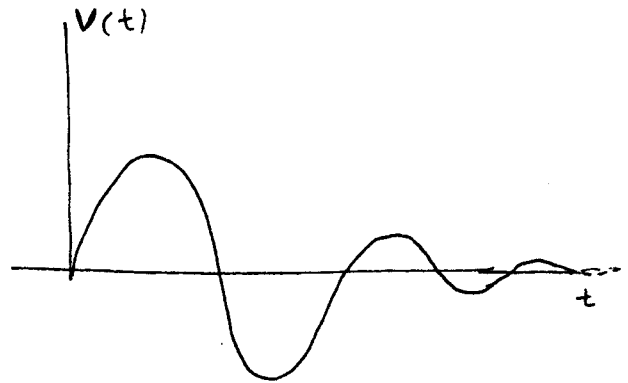
$$\begin{cases} \alpha = \frac{1}{2RC} \\ \omega_d = \sqrt{\omega_0^2 - \alpha^2} \end{cases}$$



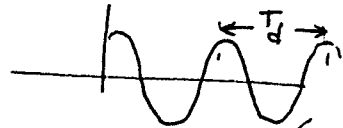
* note: If $\alpha \rightarrow 0$ ($R \rightarrow \infty$) $\Rightarrow \omega_d = \omega_0$
 $f_d = \frac{1}{T_d}$ $V(t) = B_1 \cos \omega_0 t + B_2 \sin \omega_0 t$




(c) $s_1 = s_2$ repeated roots (critically damped)

$$V(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$\alpha = \frac{1}{2RC}$$

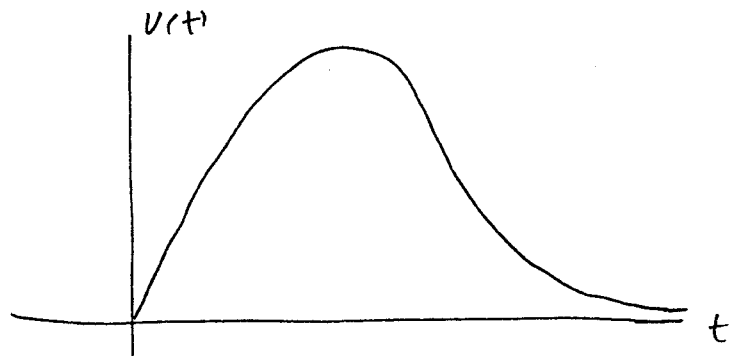

#8.2
268

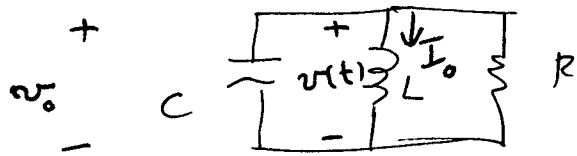

$$\begin{cases} v_0 = 0 \\ I_0 = 18 \text{ mA} \end{cases}$$

$$v(t) = 15 e^{-8000t} - 15 e^{-2000t}$$

$R, L, C = ?$

$$C \frac{dv}{dt} + \frac{1}{L} \int_0^t v(\tau) d\tau + I_0 + \frac{v}{R} = 0 \quad t=0$$

$$C \frac{dv(0)}{dt} + \frac{0.018}{R} + \frac{v(0)}{R} = 0 \quad (1)$$

$$v(t) = 15 e^{s_1 t} - 15 e^{s_2 t}$$

$$\left. \frac{dv}{dt} \right|_{t=0} = (15)(-8000) + (15)(2000) \quad (2)$$

$$(1), (2) \Rightarrow \underline{\underline{C = 0.2 \mu\text{F}}}$$

$$\begin{cases} s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \\ s_1 + s_2 = -2\alpha \\ |s_1 - s_2| = 2\sqrt{\alpha^2 - \omega_0^2} \end{cases}$$


$$s_1 + s_2 = -2\alpha = -8000 - 2000 \Rightarrow \alpha = 5000$$

$$\alpha = \frac{1}{2RC} \Rightarrow \underline{\underline{R = 500 \Omega}}$$

$$|s_1 - s_2| = 2\sqrt{\alpha^2 - \omega_0^2} = 6000 \Rightarrow \omega_0 = 4000 \frac{\text{rad}}{\text{s}}$$

$$\omega_0^2 = \frac{1}{LC} \Rightarrow \underline{\underline{L = 312.5 \text{ mH}}}$$

8.3
268

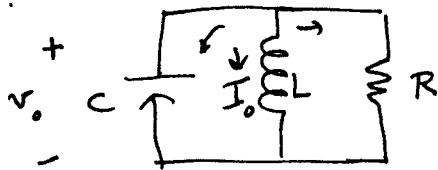

$$R = 2k$$

$$C = .25 \mu F$$

$$L = 6.25 H.$$

$$I_o = 0.$$

$$v_o = -60 V$$

a) $i_L(0^+) = 0$

$$i_R(0^+) = \frac{-60}{2k} = -30 \text{ mA}$$

$$i_C(0^+) = - (i_R(0^+) + i_L(0^+)) = 30 \text{ mA}$$

b) $\alpha = \frac{1}{2RC} = \frac{1}{2(2000)(.25 \times 10^{-6})} = 1000.$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(6.25)(.25 \times 10^{-6})} = 64 \times 10^4$$

$$\omega_0 = 800. \frac{\text{rad.}}{\text{sec}}$$

$$\alpha^2 > \omega_0^2 \quad \therefore \text{overdamped.}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \rightarrow -400. \\ \rightarrow -1600.$$

$$v(t) = A_1 e^{-400t} + A_2 e^{-1600t} \quad t \geq 0$$

$$v(0) = A_1 + A_2 = -60$$

$$i_c(0^+) = C \frac{dv(0^+)}{dt} = \frac{1}{25 \times 10^{-6}} \left[-400 A_1 - 1600 A_2 \right] = 30 \times 10^{-3} \text{ A} ; t \geq 0^+$$

$$\therefore A_1 = 20 \text{ V}$$

$$A_2 = -80 \text{ V}$$

$$\therefore v(t) = 20 e^{-400t} - 80 e^{-1600t} ; t \geq 0^+$$


$$c) \quad i_L(t) = - (i_R + i_c)$$

$$i_R = \frac{v(t)}{R} = 10 e^{-400t} - 40 e^{-1600t} \text{ mA}$$

$$i_c = C \frac{dv}{dt} = -2 e^{-400t} + 32 e^{-1600t} \text{ mA}$$

$$i_L(t) = -8 e^{-400t} + 8 e^{-1600t}, \text{ mA} ; t \geq 0^+$$

8.4 :
269

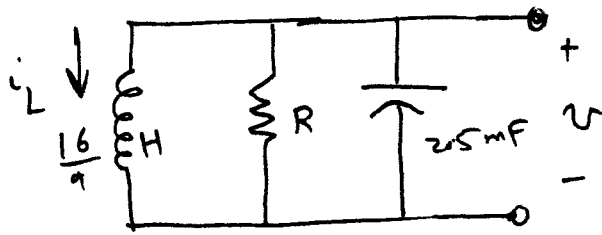

$R = ?$

$i_R(0^+)$, $i_L(0^+)$, $i_C(0^+) = ?$

$$v(t) = 50 e^{-5t} - 90 e^{-45t} \quad \text{V}; \quad t \geq 0$$

$$i_L(0^+) = ?$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \left. \begin{array}{l} \rightarrow -5 \\ \rightarrow -45 \end{array} \right\}$$

$$s_1 + s_2 = -2\alpha = -50$$

$$\alpha = 25 \text{ s} = \frac{1}{2RC} \Rightarrow R = 8 \Omega$$


$$v(0^+) = 50 - 90 = -40 \text{ A}$$

$$i_R(0^+) = \frac{-40}{8} = \underline{-5 \text{ A}}$$

$$i_C(0^+) = C \frac{dv(0)}{dt} = 2.5 \times 10^{-3} (-250 + 4050) = 9.5 \text{ A}$$

$$i_L(0^+) = -9.5 + 5 = \underline{-4.5 \text{ A}}$$

8.5
269

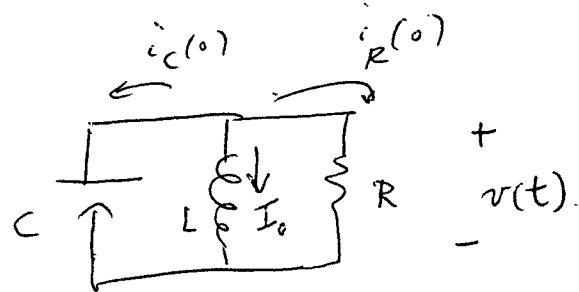

$$v = 10 e^{-\underbrace{\alpha}_{1000} t} \left(4 \cos \underbrace{5000 t}_{\omega_d} - \sin 5000 t \right)$$

$$C = 0.5 \text{ MF}$$

(a) $R = ?$

$$\alpha = 1000 = \frac{1}{2RC} \Rightarrow$$

$$R = \frac{10^6}{(2000)(0.5)}$$

$$= 1 \text{ k}\Omega$$

(b) $\omega_D = \sqrt{\omega_0^2 - \alpha^2} = 5000$

$$\omega_0^2 = 25 \times 10^6 + 10^6 = 26 \times 10^6 = \frac{1}{LC}$$

$$L = \frac{1}{(26)(10^6)(0.5)(10^{-6})} = \frac{1}{13} = 0.0769 \text{ H}$$

(c) $V_0 = v(0) = 40 \text{ V}$

(d) $I_0 = - (i_C(0) + i_R(0))$

$$i_R(0) = \frac{V_0}{R} = \frac{40}{1} = 40 \text{ mA}$$

$$i_C(0) = i_C(t) \Big|_{t=0} = C \frac{dv}{dt} \Big|_{t=0} = (0.5) \left[\dots \right] \Big|_{t=0} = -45 \text{ mA}$$

$$\therefore I_0 = -(-45 + 40) = 5 \text{ mA}$$

$$(e) \quad i_L(t) = \frac{1}{L} \int_0^t v(t) dt + I_0$$

or

$$i_L(t) = - (i_C(t) + i_R(t))$$

8.6 :
269


$$R = 5 \text{ k}$$

$$L = 8 \text{ H}$$

$$C = 0.125 \text{ } \mu\text{F}$$

$$V_0 = 30 \text{ V}$$

$$I_0 = 6 \text{ mA}$$

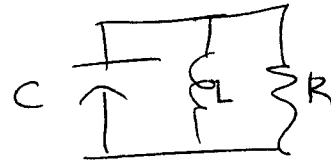

$$\textcircled{a} \quad s^2 + \frac{1}{Rc} s + \frac{1}{Lc} = 0$$

$$s^2 + \frac{1}{(5 \times 10^3)(.125)(10^{-6})} s + \frac{1}{(8)(.125)(10^{-6})} = 0$$

$$s^2 + 1600 s + 1000000 = 0$$

$$s_{1,2} = -800 \pm \sqrt{(800)^2 - 1000000} = \underbrace{-800 \pm j600}_{-\alpha \pm j\omega_d}$$

$$v(t) = e^{-800t} [B_1 \cos 600t + B_2 \sin 600t]$$

$$B_1 = v(0) = \underline{\underline{30 \text{ V}}}$$

$$v'(0) = -\frac{1}{C} \left(\frac{V_0}{R} + I_0 \right) = \omega_d B_2 - \alpha B_1 \Rightarrow \underline{\underline{B_2 = -120}}$$

$$v(t) = 30e^{-800t} (C_1 \cos 600t - 4 \sin 600t) ; t \geq 0$$

$$(b) \quad \frac{dv}{dt} = 0 \implies \tan 600t = \frac{32}{26}$$

$$\therefore 600t = \tan^{-1} \frac{32}{26} = (50.91^\circ + k\pi)^\circ$$

$$k = 0, \pm 1, \pm 2, \dots$$

$$= 0.8885 + k\pi \quad \text{radians}, \quad k = 0, 1, 2, \dots$$

$$t_1 = \frac{0.8885}{600} = 1480.8 \mu\text{s}$$


$$t_2 = 6716.79 \mu\text{s}$$

$$t_3 = 11952.78 \mu\text{s}$$

$$(c) \quad \omega_d = 600 = \frac{2\pi}{T_d} \implies T_d = \frac{2\pi}{600} = t_3 - t_1$$



8.7
269

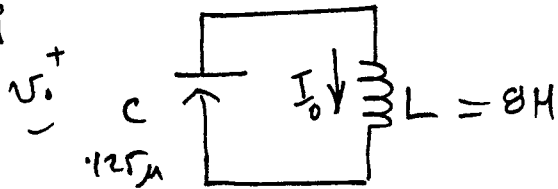

a) $v_s = 30 \text{ V}$ $\omega_s = 1000$
 $I_0 = 6 \text{ mA}$

$R = \infty, \alpha = 0 \Rightarrow s_{1,2} = \pm j\omega_0 = \pm j1000.$

$v(t) = B_1 \cos 1000t + B_2 \sin 1000t$

$v(0^+) = B_1 = 30 \text{ V}$

$\frac{dv(0^+)}{dt} = -48000 = 1000 B_2 \Rightarrow B_2 = -48 \text{ V}$

$C \frac{dv(0)}{dt} = -I_0 \Rightarrow \frac{dv(0)}{dt} = -\frac{I_0}{C}$
 $= -\frac{6 \times 10^{-3}}{125 \times 10^{-6}}$

$v(t) = 30 \cos 1000t - 48 \sin 1000t ; t \geq 0$

b) $2\pi f = 1000 \therefore f = 159.15 \text{ Hz.}$

c) $\frac{dv}{dt} = -35000 \sin 1000t - 48000 \cos 1000t = 0$

$t_e 1000t = -1.6 \Rightarrow 1000t = 1.22 + 180k$

$|V_{\max}| = |30 \cos 1.22 - 48 \sin 1.22| = 56.6 \text{ V}$